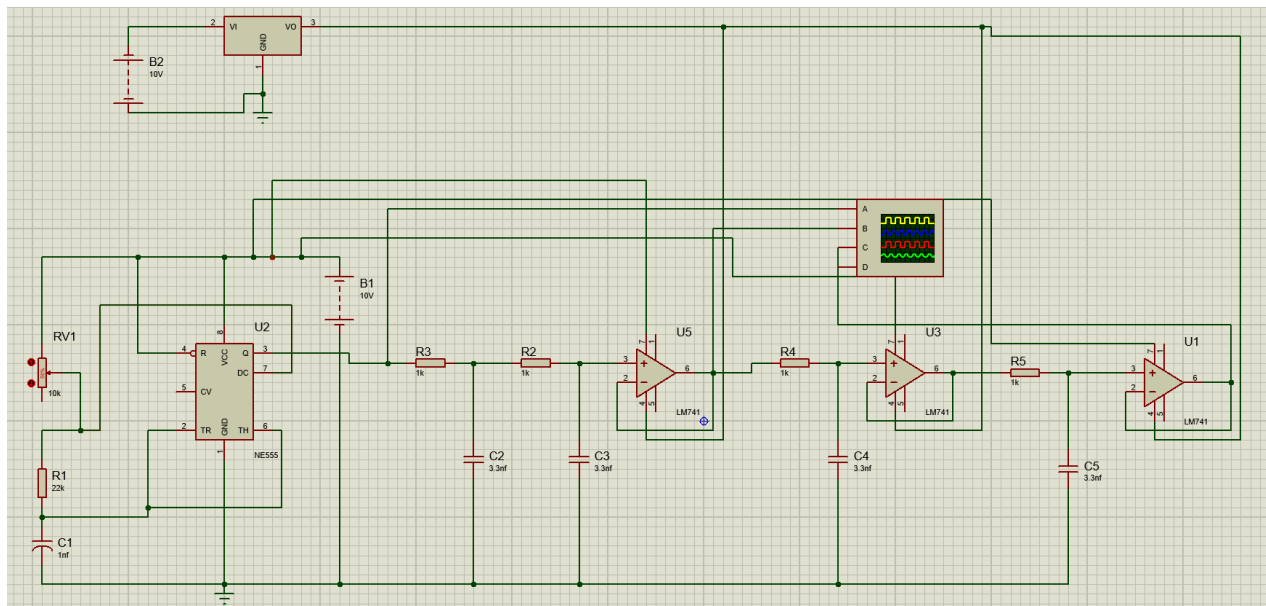


# Function Generator (TIMER 555)



Name: Moatasem Osama

## Objective:

The goal of this project is to design and construct a function generator capable of producing three distinct waveforms **square**, **triangle**, and **sin**.


Using an NE555 timer as the square wave source, an **integrator** op-amp to convert the square wave to a triangle wave, and a series of low-pass filter stages using LM741 op-amps to transform the triangle wave into a sine wave.

The generator will operate at an adjustable frequency around 30 kHz with an output amplitude of approximately  $\pm 10$  V, suitable for educational demonstrations, signal testing, and basic electronic applications.

## System Overview:

The function generator consists of three main stages:

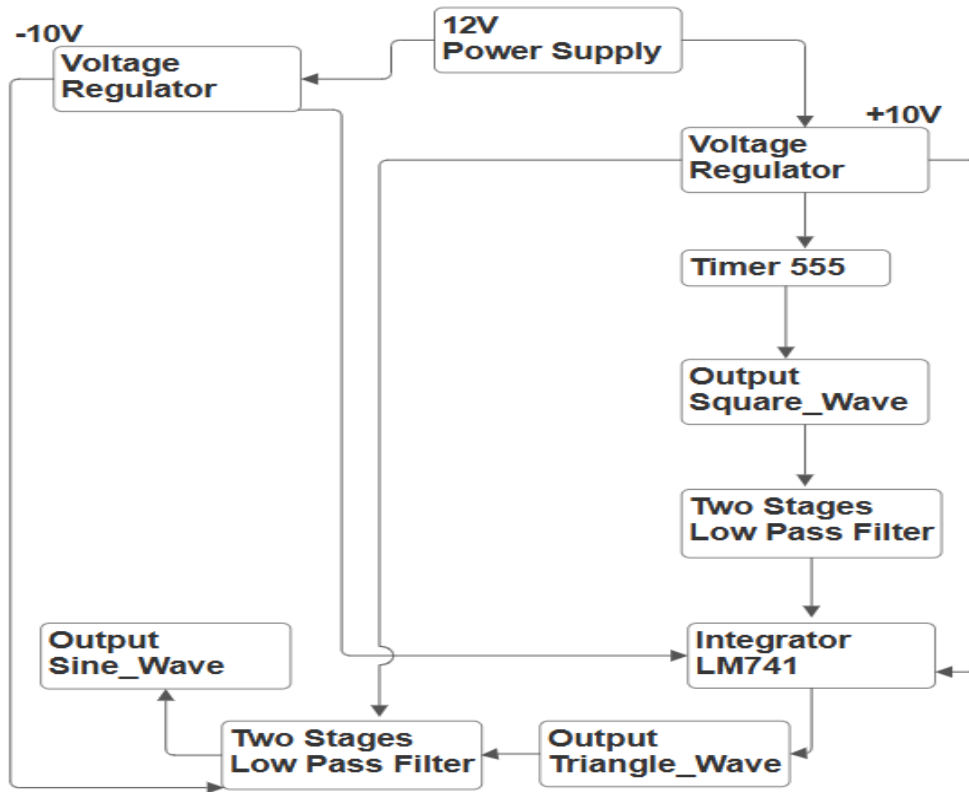1. **Square Wave Generation:** An NE555 timer configured as an astable multivibrator produces a square wave with a peak amplitude of  $\pm 10$  V and an adjustable frequency around 30kHz.
2. **Triangle Wave Generation:** An LM741 op-amp configured as an integrator converts the square wave into a triangle wave by integrating the input signal.
3. **Sine Wave Generation:** Two additional LM741 op-amps, configured as low-pass filters in a Sallen-Key topology, smooth the triangle wave into a sine wave by attenuating higher harmonics.



Range of Frequency  $\rightarrow \sim 30\text{ kHz}$

$$R_a = 5\text{ k}\Omega, R_b = 77\text{ k}\Omega, C = 1\text{ nF}$$

assume  $\Rightarrow R_a = 5\text{ k}\Omega$

$$18.738\text{ }\mu\text{s}$$

$$15.268\text{ }\mu\text{s}$$

$$T_{on} = 0.694(5000 + 77000) \times 1 \times 10^{-9} = 18.738\text{ }\mu\text{s}$$

$$T_{off} = 0.694(77000) \times 1 \times 10^{-9} = 15.268\text{ }\mu\text{s}$$

$$\text{Duty cycle} = \frac{T_{on}}{T_{on} + T_{off}} = \frac{18.738}{18.738 + 15.268} \times 100 = 55\%$$

$$T = 0.694(R_a + 2R_b)C = 0.694(5000 + 144000) \times 1 \times 10^{-9}$$

$$T = 34\text{ }\mu\text{s}$$

$$\Rightarrow f = 1/T = 29406.7\text{ Hz} \sim 30\text{ kHz}$$

Anal: P, t...

## RC filter (low Pass)

$$f = \frac{1}{2\pi RC}$$



assume  $R = 1k\Omega$  at  $f = 41.21\text{Hz}$


$$C = 3.86\text{nF}$$

M741

$$R_2 = R_1 = 0\Omega$$

$$G = 1$$

unit gain

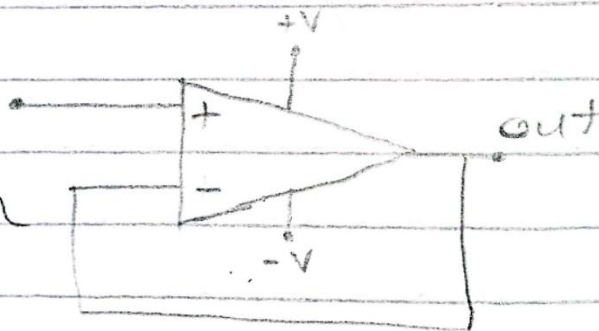

first stage  $\rightarrow$  integrator

second "  $\rightarrow$  low Pass filter

third "  $\rightarrow$  low Pass filter

## Power Calculations:

### Power Calculations

#### 1) LM 7810 Regulator:

$V_{in} = 12V$ ,  $V_o = 10V$ , Typical of signal generation  
The load current = 10mA

From Data sheet

$$I_{quiescent\ current} = 8mA$$

$$P_{in} = 12 \times (0.1 + 0.008) = 1.296\text{ Watt}$$

$$P_{out} = 10V \times 0.1 = 1\text{ Watt}$$

$$P_{diss} = 1.296 - 1 = 0.296\text{ Watt}$$

#### 2) Timer

Typical Current for No load = 3mA

$$P = 10V \times 0.003 = \underline{\underline{0.03\text{ Watt}}}$$

### 3) LM741 OP. Amp

Supply  $\rightarrow \pm 10V$

From Data sheet Power Cons. = 85mWatt

$\hookrightarrow$  in Max.

Power for 3 op. amps =  $3 \times 85mW = \underline{\underline{0.255Watt}}$

Total Power Consumption =  $1.296 + 0.03 + 0.255$   
 $= \underline{\underline{1.581Watt}}$